

# EE 2420 Lab Guide 5: 3-Bit Counter State Machine

*Written By: Grant Seligman, Gabe Garves, James Starks*

## Example Overview:

Design a state machine that follows this sequence:

000 → 100 → 110 → 111 → 101 → 001 → 011 → 010 → 000 ... {Gray code}

The data bit can be interpreted as a clock signal. If the data bit is high, we proceed to the next or previous step depending on the direction bit. If the data bit is low, output doesn't change. When the direction bit is set to 0, the sequence should follow the order above. When the direction bit is set to 1, the sequence should go in the reverse order. There must also be a reset bit that resets the state machine. When reset goes low the state machine should be forced into the 000 state, otherwise normal operation will continue. Figure 1 is the example 3-bit state machine we will be working with.

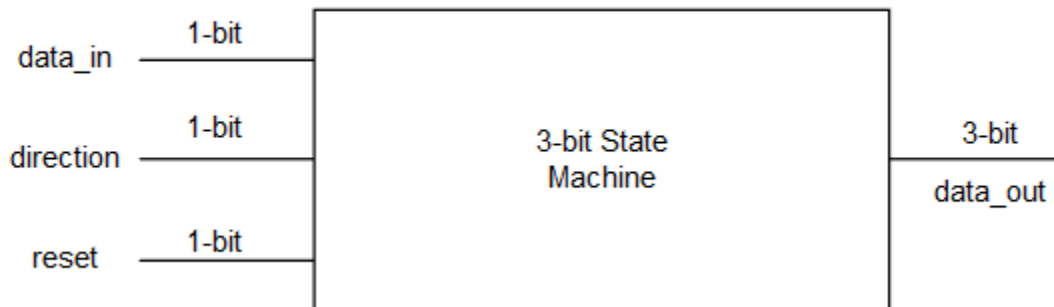


Figure 1

## Verilog Code Breakdown:

For each state, a value is being assigned to the output. Since we are assigning values to the output, we have to define the output as a register to hold these values. We must also create/declare a variable/register named state to keep track of the current state. Whenever the direction or data bit goes high, (posedge) or the reset goes low, (negedge) the always block executes. If reset is ever low, the state is reset and the rest of the always block is ignored. The direction bit determines which section of the always block executes and will increment the state value accordingly. The current state and data bit will determine the next state. The case statement at the end executes every time the always block does, and sets the output to the next state. Not shown in **Figure 1**, is the clock input signal needed to drive the states. One can use the Clock Converter module from the counter lab to create a slow enough clock to see each state.

```

1 // State Machine
2 /*
3  AUTHOR: James Starks
4  DATE: 11/15/2019
5  FROM: TXST SENIOR DESIGN PROJECT FALL 2019
6  FOR: TEXAS STATE UNIVERSITY STUDENT AND INSTRUCTOR USE
7  */
8 // RTL Code
9
10 module state_machine(out, dir, rst, clk);
11
12     // Store out value using 3 bits
13     // This is where
14     output reg [2:0] out;
15
16     // State machine control signals
17     input dir, rst, clk;
18
19     // Assigned output states to have manageable names
20     parameter s0 = 3'b000;
21     parameter s1 = 3'b100;
22     parameter s2 = 3'b110;
23     parameter s3 = 3'b111;
24     parameter s4 = 3'b101;
25     parameter s5 = 3'b001;
26     parameter s6 = 3'b011;
27     parameter s7 = 3'b010;
28
29     // Enter at every positive edge of clk
30     always@(posedge clk) begin
31
32         // If rst is high, return to state s0
33         if (rst)
34             out = s0;
35
36         // Check current state and if dir = 0 increment state, if dir = 1 decrement state
37         case(out)
38
39             s0: if(!dir) out = s1;
40                  else out = s7;
41
42             s1: if(!dir) out = s2;
43                  else out = s0;
44
45             s2: if(!dir) out = s3;
46                  else out = s1;
47
48             s3: if(!dir) out = s4;
49                  else out = s2;
50
51             s4: if(!dir) out = s5;
52                  else out = s3;
53
54             s5: if(!dir) out = s6;
55                  else out = s4;
56
57             s6: if(!dir) out = s7;
58                  else out = s5;
59
60             s7: if(!dir) out = s0;
61                  else out = s6;
62
63         endcase
64
65     end
66
67 endmodule
68

```

Figure 2

The direction bit is set to active low and will reverse the states when switched high. What is nice about this state machine is that it is almost identical to the counter except now one can control the direction of states.

## FPGA Implementation:

Using your knowledge from the previous labs, implement your verilog code into a **symbol** for each module. For this project, along with the module in **Figure 2**, we will just use the 12Mhz clock and drop it down to a 5Hz clock to see the changes in state easier. All that changes is the number of counts per cycle:


$$12E6 / 5 = 2400000 \text{ counts per cycle}$$

```
11 // Clock Converter: 12MHz to 5Hz
12 /*
13  AUTHOR: Grant Seligman
14  DATE: 02/10/2020
15  FROM: TXST SENIOR DESIGN PROJECT FALL 2019-SPRING 2020
16  FOR: TEXAS STATE UNIVERSITY STUDENT AND INSTRUCTOR USE
17  ORIGINAL CODE SOURCE:
18  https://electronics.stackexchange.com/questions/202876/
19  how-can-i-generate-a-1-hz-clock-from-50-mhz-clock-coming-from-an-altera-board
20  */
21 module FiveHzClock(clkout, clkkin); //ports
22
23  output reg clkout;
24  input clkkin;
25  reg [23:0] counter; //need at least 24 bits
26
27  initial //happens first and only once
28  begin
29      counter = 0;
30      clkout = 0;
31  end
32  //Counts down until it reaches zero then resets
33  always @(posedge clkkin)
34  begin
35      if (counter == 0)
36      begin
37          counter <= 2399999; //Blocking statement. Remember you start counting at zero.
38          clkout <= ~clkout; //Blocking statement. ~clkout is the same as !clkout
39          end
40      else
41      begin
42          counter <= counter -1; //Blocking statement
43          end
44      end
45  endmodule
```

**Figure 3**


*The original code for the counter was sourced from a stackexchange webpage. [1] The module was modified by Grant Seligman.*

Make sure to set the finished .bdf file as your Top Level Entity before compiling and then setting the pins. This sets the entire block chain as one entity and allows Quartus to set up the pin planner correctly. Follow Figures 5 - 7 to set the Top-Level Entity.

 


**Figure 5**

Go to the **Project Navigator** and use the drop down menu and select **Files**. This will show you all the current files within your Quartus Project.

 

**Figure 6**

Right-click on the .bdf file of your project and select **Set as Top-Level Entity**.

 

**Figure 7**

Your **.bdf** file should look similar to **Figure 8**. Then follow **Table 1** and **Figure 9** to set your pins accordingly. You can simplify the process if you use a function generator as a clock input, but you will have to set the **clk** input to an orange pin.

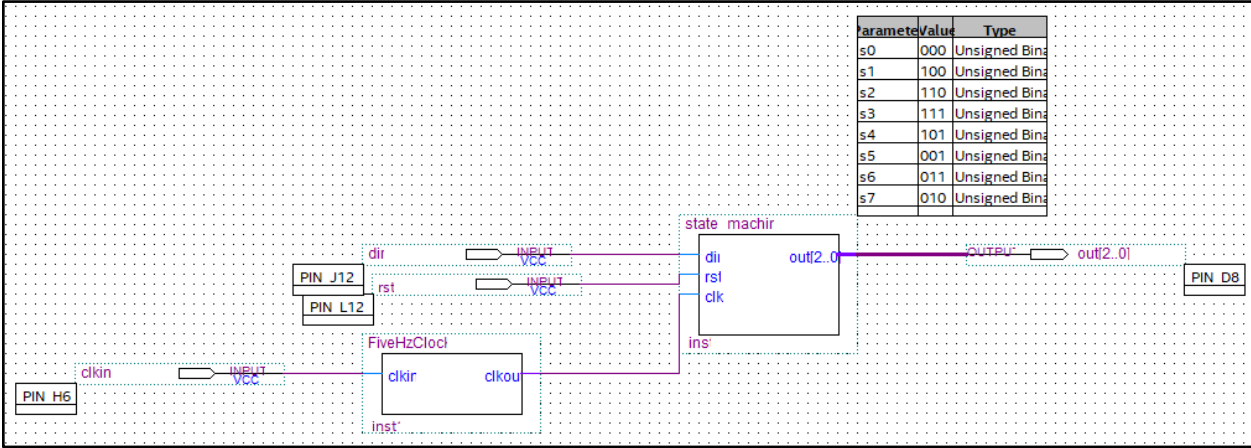


Figure 8

Node Name	Direction	Location	I/O Standard
rst	Input	PIN_L12	3.3-V LVTTL
clkir	Input	PIN_H6	3.3-V LVTTL
dir	Input	PIN_J12	3.3-V LVTTL
out[2]	Output	PIN_C9	3.3-V LVTTL
out[1]	Output	PIN_C10	3.3-V LVTTL
out[0]	Output	PIN_D8	3.3-V LVTTL

Table 1

# TEI0001-02 MAX1000


 


Figure 9

Working with the Peripheral Board

 

For the board, all one needs is two dip switches to control reset and the direction. Depending on how you set your pins your board should look similar to **Figure 10**.



**Figure 10**

## REFERENCES SECTION

- [1] “verilog - How can I generate a 1 Hz clock from 50 MHz clock coming from an Altera board?,” *Electrical Engineering Stack Exchange*. [Online]. Available: <https://electronics.stackexchange.com/questions/202876/how-can-i-generate-a-1-hz-clock-from-50-mhz-clock-coming-from-an-altera-board>. [Accessed: 10-Feb-2020].